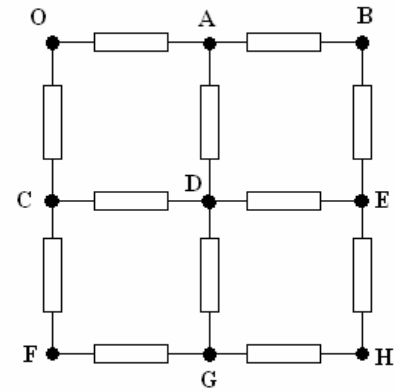


ENGINEERING SCIENCE C103
EXAM SOLUTIONS 2005

Q 7 Twelve 10 kΩ resistors are connected as shown.

Determine the voltage at each node if:-

- a) a 6 V battery is connected between O and B
- b) a 6 V battery is connected between O and H



a) Because of symmetry the voltage at A D and G must be 3 V

Examining node C we may deduce the current flow is as shown since V_C must be less than 3 V

Working in mA, Ohms Law gives

$$I_1 = V_C/10K = 0.1 V_C$$

$$I_2 = (3 - V_C)/20k = 0.15 - 0.05 V_C$$

$$I_3 = (3 - V_C)/10k = 0.3 - 0.1 V_C$$


Kirchoff's rule gives

$$I_1 = I_2 + I_3$$

$$0.1 V_C = 0.15 - 0.05 V_C + 0.3 - 0.1 V_C$$

$$0.25 V_C = 0.45$$

$$V_C = 1.8 V$$

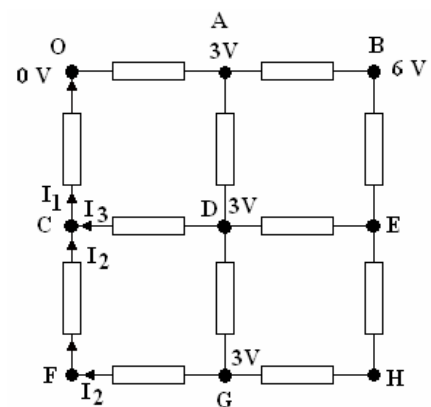

$$I_1 = 0.18 \text{ mA}$$

$$I_2 = 0.06 \text{ mA}$$

$$I_3 = 0.12 \text{ mA}$$


We can easily deduce the other currents as shown

Now use Ohms Law to find voltages.

$$V_F = 3 - 0.06 \times 10 = 2.4 V$$

$$V_E = 6 - 0.18 \times 10 = 4.2 V$$

$$V_H = 3 + 0.06 \times 10 = 3.6 V$$

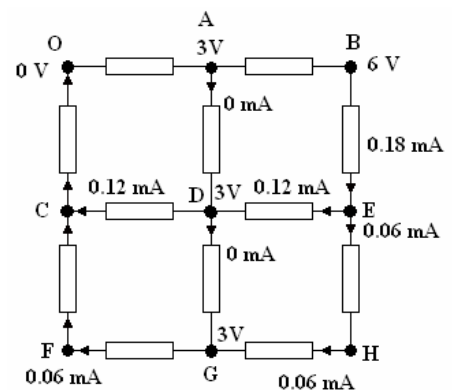

b) Again by symmetry we can deduce that V_G , V_D and V_A are 3V

Again examining node C we deduce the voltage is between 3 and 0 so the currents flow as shown.

$$I_1 = V_C/10K = 0.1 V_C$$

$$I_2 = (3 - V_C)/10k = 0.3 - 0.1 V_C$$

$$I_3 = (3 - V_C)/10k = 0.3 - 0.1 V_C$$

Kirchoff's rule gives

$$I_1 = I_2 + I_3$$

$$0.1 V_C = 0.3 - 0.1 V_C + 0.3 - 0.1 V_C$$

$$0.3 V_C = 0.6 \quad V_C = 2 V$$

By symmetry $V_A = 2 V$

$$I_1 = 0.2 \text{ mA} \quad I_2 = 0.1 \text{ mA} \quad I_3 = 0.1 \text{ mA}$$

Now use Ohms Law to find voltages.

$$V_G = 3 + 0.1 \times 10 = 4 V$$

By symmetry $V_E = 4 V$

